


Chapter 8 Parallel Circuits

In-Class Questions

Prerequisite Concepts:

- **Kirchoff's Junction Rule:** current into junction equals current out


Questions #1–6 refer to this diagram:

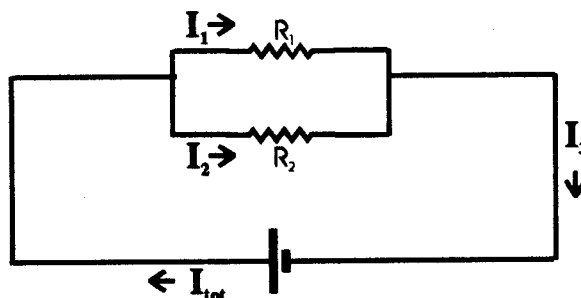

- As shown in the diagram, I_{tot} refers to the current flowing out of the battery. How does the magnitude of I_3 compare to that of I_{tot} ?
 - $I_3 > I_{tot}$
 - $I_3 = I_{tot}$
 - $I_3 < I_{tot}$
 - answer depends on the magnitudes of R_1 and R_1
 - answer depends on the magnitude of the battery voltage
- How does the magnitude of I_1 compare to that of I_{tot} ?
 - $I_1 > I_{tot}$
 - $I_1 = I_{tot}$
 - $I_1 < I_{tot}$
 - answer depends on the magnitudes of R_1 and R_1
 - answer depends on the magnitude of the battery voltage
- Let ΔV_{R_1} represent the *magnitude* of the potential difference between the two sides of resistor R_1 . How does ΔV_{R_1} compare to the magnitude of the battery voltage, ΔV_{bat} ?
 - $\Delta V_{R_1} > \Delta V_{bat}$
 - $\Delta V_{R_1} = \Delta V_{bat}$
 - $\Delta V_{R_1} < \Delta V_{bat}$
 - answer depends on magnitude of R_1
 - answer depends on relative magnitudes of R_1 and R_2

4. Let ΔV_{R_2} represent the *magnitude* of the potential difference between the two sides of resistor R_2 . How does ΔV_{R_2} compare to the magnitude of the battery voltage, ΔV_{bat} ?
- $\Delta V_{R_2} > \Delta V_{bat}$
 - $\Delta V_{R_2} = \Delta V_{bat}$
 - $\Delta V_{R_2} < \Delta V_{bat}$
 - answer depends on magnitude of R_1
 - answer depends on relative magnitudes of R_1 and R_2
5. If $R_1 = R_2$, how do the currents through the resistors compare?
- $I_1 > I_2$
 - $I_1 = I_2$
 - $I_1 < I_2$
 - answer depends on the magnitude of the battery voltage
6. If $R_1 > R_2$, how do the currents through the resistors compare?
- $I_1 > I_2$
 - $I_1 = I_2$
 - $I_1 < I_2$
 - answer depends on the magnitude of the battery voltage

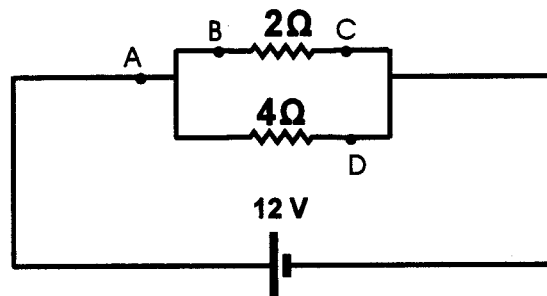Questions #7–15 refer to the diagram below. Assume that the magnitude of the electric potential at the *negative* terminal of the battery is 0 volts.




7. What is the magnitude of the electric potential at point A?
- 0 V
 - 3 V
 - 4 V
 - 6 V
 - 8 V
 - 12 V

8. What is the magnitude of the electric potential at point B?
- A. 0 V
 - B. 3 V
 - C. 4 V
 - D. 6 V
 - E. 8 V
 - F. 12 V
9. What is the magnitude of the electric potential at point C?
- A. 0 V
 - B. 3 V
 - C. 4 V
 - D. 6 V
 - E. 8 V
 - F. 12 V
10. What is the magnitude of the electric potential at point D?
- A. 0 V
 - B. 3 V
 - C. 4 V
 - D. 6 V
 - E. 8 V
 - F. 12 V
11. What is the value of $I_{4\Omega}$, i.e., the magnitude of current flow through the 4Ω resistor?
- A. 3 A
 - B. 4 A
 - C. 6 A
 - D. 8 A
 - E. 9 A
 - F. 12 A

12. What is the value of $I_{2\Omega}$, i.e., the magnitude of current flow through the 2Ω resistor?
- A. 3 A
 - B. 4 A
 - C. 6 A
 - D. 8 A
 - E. 9 A
 - F. 12 A
13. What is the magnitude of current flowing past point B?
- A. 3 A
 - B. 4 A
 - C. 6 A
 - D. 8 A
 - E. 9 A
 - F. 12 A
14. What is the magnitude of current flowing past point D?
- A. 3 A
 - B. 4 A
 - C. 6 A
 - D. 8 A
 - E. 9 A
 - F. 12 A
15. What is the magnitude of I_{tot} ?
- A. 3 A
 - B. 4 A
 - C. 6 A
 - D. 8 A
 - E. 9 A
 - F. 12 A

In-Class Exercises

Questions #1–4 refer to this figure:

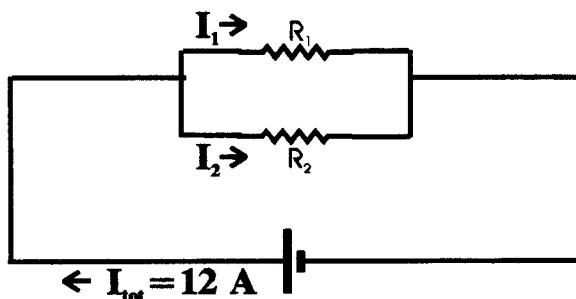

Let I_1 and I_2 represent the current flowing through resistors R_1 and R_2 , respectively. $I_{tot} = 12 \text{ A}$, as indicated.

1. What is the value of $(I_1 + I_2)$?

$$(I_1 + I_2) = \underline{\hspace{2cm}}$$

2. If $R_2 = R_1$, find the following values:

$$\frac{I_1}{I_2} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$

3. If $R_2 = 2R_1$, find the following values:

$$\frac{I_1}{I_2} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$


4. If $R_2 = 3R_1$, find the following values:

$$\frac{I_1}{I_2} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$

Questions #5–7 refer to this diagram:

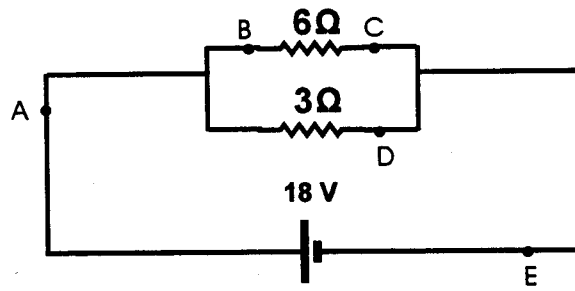

5. Assume that the potential at the negative terminal of the battery is 0 volts. Indicate the potential at the following points:

A: _____

B: _____

C: _____

D: _____

E: _____

6. Write down the magnitude of the following potential differences:

A. $\Delta V_{AC} =$ _____

B. $\Delta V_{BE} =$ _____

C. $\Delta V_{CE} =$ _____

D. $\Delta V_{DA} =$ _____

E. $\Delta V_{BD} =$ _____

7. Write down the amount of current flowing past the following points in the circuit:

A: _____

B: _____


C: _____

D: _____

E: _____



Homework Exercises

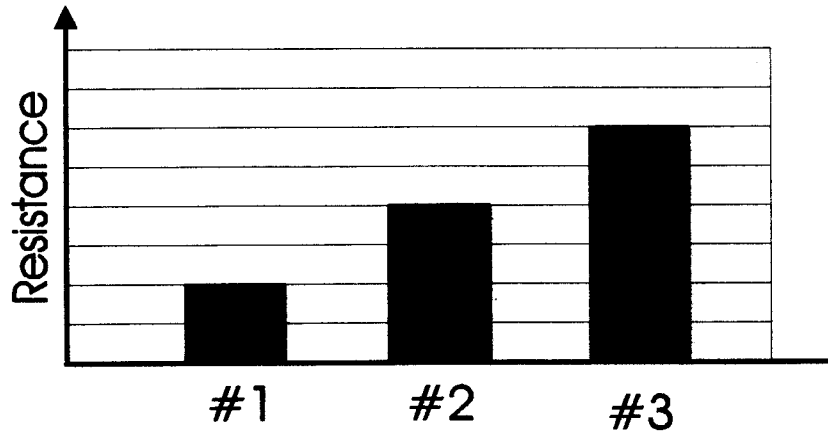1. Three resistors are connected in parallel to a battery. The bar graph below shows the relative magnitudes of the three resistances.







On the bar graphs below, draw:

- three bars, representing the relative magnitudes of the current passing through each resistor, and a fourth bar indicating the relative magnitude of the current flowing through the battery (this is the “total current in the circuit”).
- three bars, representing the relative sizes of the potential changes experienced by the current as it flows across each resistor, and a fourth bar indicating the relative size of the potential change experienced by the current as it flows between the terminals of the battery. Indicate increasing potential as a *positive* change, and decreasing potential as a *negative* change.

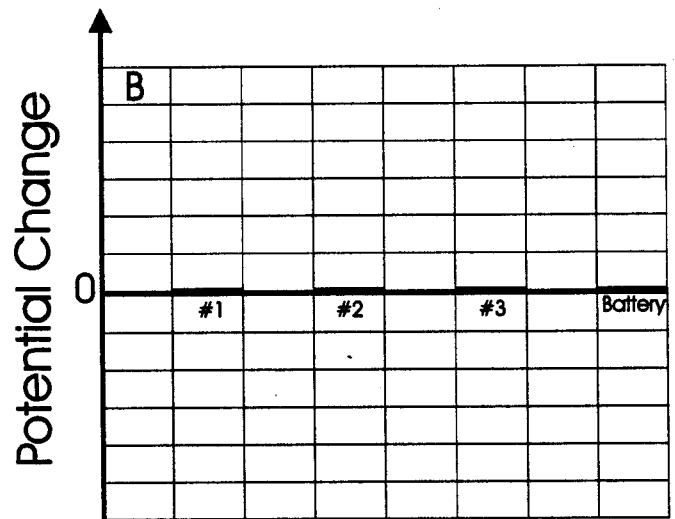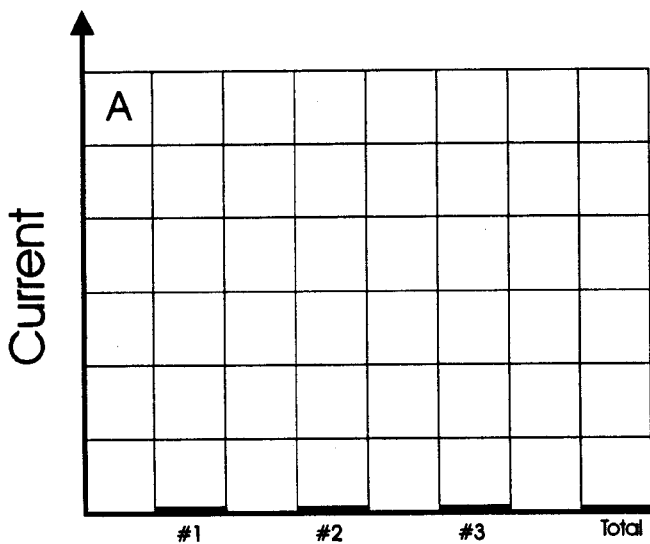

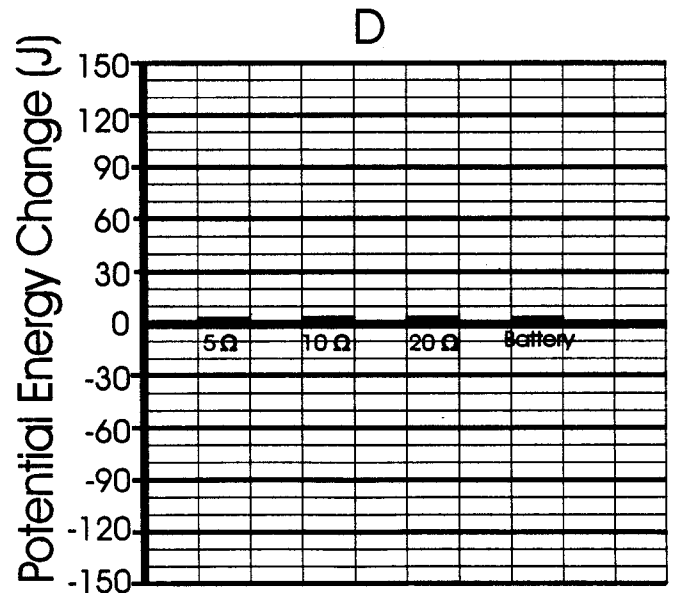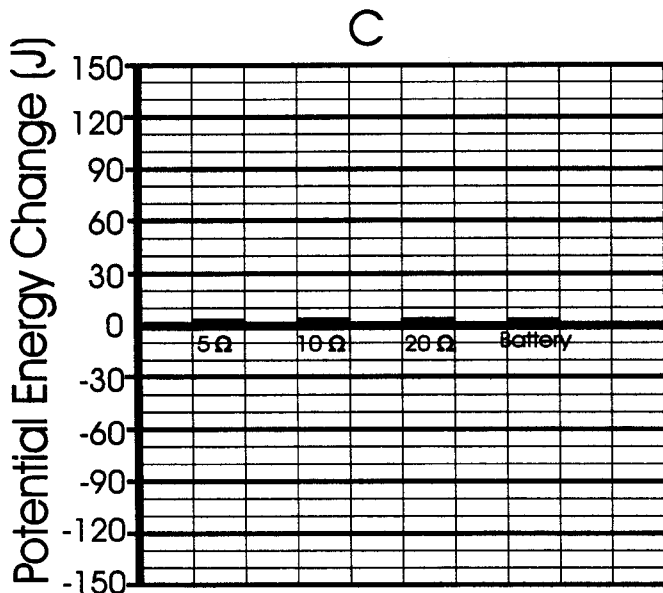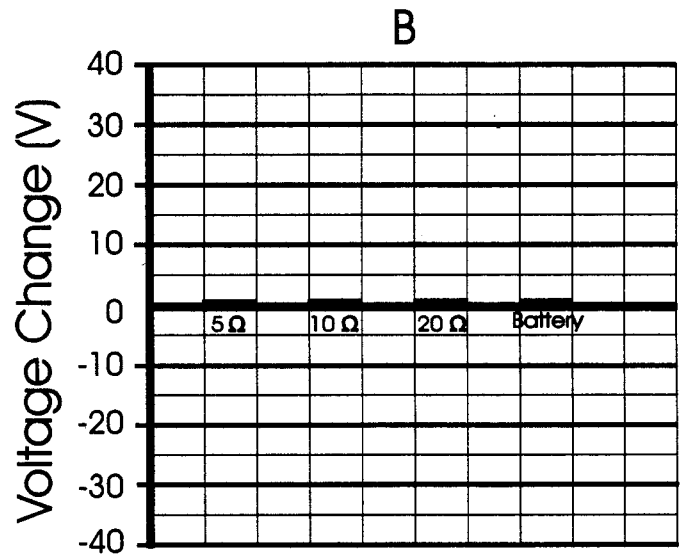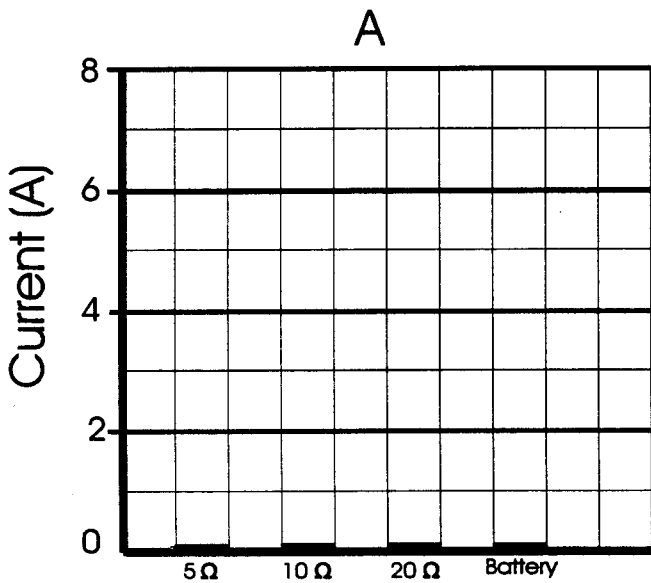2. A 5-ohm resistor, a 10-ohm resistor and a 20-ohm resistor are connected in parallel with a 20-V battery. (Each of the following bar graphs should have four bars.)
- Draw a bar graph showing the current flowing through the 5-ohm resistor, the 10-ohm resistor, the 20-ohm resistor, and the battery.
 - Draw a bar graph showing the potential changes experienced by the current as it flows around the circuit. Indicate the potential increase (positive) or decrease (negative) across the 5-ohm resistor, the 10-ohm resistor, and the 20-ohm resistor, and between the terminals of the battery.
 - Draw a bar graph showing the amount of potential energy gained (positive change) or lost (negative change) by a 2-C charge as it goes through the 5-ohm resistor, the 10-ohm resistor, the 20-ohm resistor, and the battery.
 - Repeat C, this time assuming the battery is 40 V.



3. A $2\text{-}\Omega$ and a $4\text{-}\Omega$ resistor are connected in parallel to a battery. $\Delta V_4 = 12\text{ V}$. $\Delta V_{\text{bat}} = ?$
Explain your answer.

4. A $3\text{-}\Omega$ and a $5\text{-}\Omega$ resistor are connected in parallel to a battery. $I_{3\Omega} = 6\text{ A}$. $\Delta V_{\text{bat}} = ?$
Explain your answer.