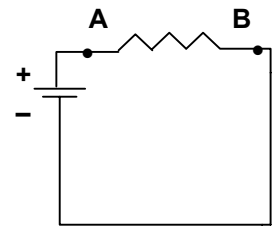


## Electric Power: Energy Changes in Circuits



1. Consider the circuit shown in the diagram. Let us suppose that a current  $I$  is flowing in this circuit. What is the definition of current, in terms of charge and time?

$$I =$$

2. Let's consider the current as it flows between point A and point B. Draw an arrow on the circuit to indicate the direction of flow of a conventional current of positive charges.
3. In the time  $\Delta t$ , we will say that a quantity of charge equal to  $\Delta q$  flows past point A. How much charge will flow past point B in the same amount of time?
4. As it flows between points A and B, what will happen to the potential energy of this quantity of charge? Will it *increase, decrease, or remain the same*?
5. We have already learned that the average *kinetic energy* of this charge will not change. Will the *total energy* of this charge *increase, decrease, or remain the same*?
6. If your answer to #5 was "increase," where does the extra energy come from? If your answer was "decrease," where does the lost energy go?
7. In terms of  $V_A$  and  $V_B$  (the potential at points A and B), what will be the change in potential of the charge as it moves between points A and B? Use absolute value symbols (vertical lines) to express this as a positive quantity.
8. What will be the change in the *potential energy* of this charge as it flows between points A and B?

$$\Delta PE =$$

Is this an *increase, a decrease, or no change* in the charge's PE?

9. Consider the amount of *energy change per unit time* of the charge  $\Delta q$ . What is the name given to the quantity "*energy change per unit time*"?
10. Let's use the symbol "P" for the quantity "energy change per unit time." Use algebraic symbols to express the fact that "P" equals "energy change per unit time." Use the symbol " $\Delta TE$ " to represent "energy change."

11. Explain why  $\Delta TE = \Delta PE$  for the charge  $\Delta q$ . Rewrite your algebraic expression from #10 in terms of  $\Delta PE$ .
12. We would like to find a mathematical expression for the “energy change per unit time” in terms of the current  $I$  and the given values of the potential,  $V_A$  and  $V_B$ . In #11, you wrote down an expression for the energy change per unit time in terms of  $\Delta PE$ . Use your result from #8 to write this in terms of  $V_A$  and  $V_B$ .
13. Now use your definition of  $I$  from #1 to write your expression from #12 in terms of  $I$  and  $V_A$  and  $V_B$ .
14. Write down in words the meaning of the algebraic expression you obtained in #13. Use only words; no mathematical symbols.
15. Now consider the current as it flows through the battery. Suppose the potential difference between the terminals of the battery is  $\Delta V_{\text{bat}}$  (this is called the battery “voltage”). What is the change in potential energy of the charge  $\Delta q$  as it flows from the negative battery terminal, to the positive battery terminal? Is this an increase, a decrease, or no change?

$$\Delta PE =$$

16. Using the same argument that we went through for the flow through the resistor, write down an expression for the *amount of energy supplied by the battery per unit time*. Use the symbol “ $P$ ” to represent this quantity.
17. Write down in words the *meaning* of the algebraic expression you obtained in #16. Do not use any mathematical symbols.
18. In the case of the resistor, you can use Ohm’s law to write your result from #13 in terms of  $I$  and  $R$ , **or** in terms of  $R$ ,  $V_A$  and  $V_B$ . Do this (i.e., write two new equations), and explain why you can **not** use these equations when considering the flow through the battery itself.