

Physics 112
Quiz #14
October 15, 1999

Name: _____

IF YOU WANT A QUESTION GRADED OUT OF THREE POINTS (-1 [MINUS ONE] FOR WRONG ANSWER!!) WRITE "3" IN SPACE PROVIDED ON EACH QUESTION.

$$e = 1.60 \times 10^{-19} \text{ C}$$

- A proton is located at (-1 m, 0 m) and two protons are located at (+1 m, 0 m). A 1-C charge is located at the origin. What is the magnitude of the *net electrical force* experienced by the charge at the origin?
 - 0 N
 - 0.36×10^{-9} N
 - 0.72×10^{-9} N
 - 1.08×10^{-9} N
 - 1.44×10^{-9} N
 - 2.88×10^{-9} N
 - 4.32×10^{-9} N
- A three-ohm resistor and a four-ohm resistor are connected in series to a battery. In a separate circuit, a three-ohm resistor and a four-ohm resistor are connected in parallel to a battery with the *same* battery voltage as in the first circuit. Which resistor will have the *largest* amount of current flowing through it?
 - The three-ohm resistor in the series circuit.
 - The four-ohm resistor in the series circuit.
 - The three-ohm resistor and the four-ohm resistor in the series circuit, which have the *same* amount of current flowing through them.
 - The three-ohm resistor in the parallel circuit.
 - The four-ohm resistor in the parallel circuit.
 - The three-ohm resistor and the four-ohm resistor in the parallel circuit, which have the *same* amount of current flowing through them.

Grade out of 3? Write "3" here: _____

- Resistor A has twice the resistance of resistor B. They are connected in parallel to a battery. Then:
 - Resistor A dissipates four times as much power as resistor B.
 - Resistor A dissipates twice as much power as resistor B.
 - Resistor A dissipates the same amount of power as resistor B
 - Resistor A dissipates half as much power as resistor B.
 - Resistor A dissipates one fourth as much power as resistor B.
- A 10-ohm and a 5-ohm resistor are connected in parallel to a battery as shown in the diagram. The power dissipated in the 5-ohm resistor is P_5 . What will happen to P_5 if the *10-ohm* resistor is removed, and another resistor with resistance *less* than 5 ohms is put in its place? (No other changes are made to the circuit.)

Then P_5 :

- will increase.
- will decrease.
- will remain equal to 0 W.
- will not change, but is not equal to 0 W.
- might increase, decrease, or remain the same, depending on the precise value of the new resistance.

Grade out of 3? Write "3" here: _____

