Physics 112 Quiz #15 October 23, 2000

Name:

IF YOU WANT A QUESTION GRADED OUT OF THREE POINTS (-1 [MINUS ONE] FOR WRONG ANSWER!!) WRITE "3" IN SPACE PROVIDED ON EACH QUESTION.

1. Two identical resistors are connected in parallel to a battery. If a third resistor is added in parallel, what will happen to the total amount of energy provided each second by the battery to the circuit:

A. It will increase.

- B. It will decrease.
- C. It will remain unchanged.
- D. It will depend on whether the third resistor has a resistance larger than, smaller than, or equal to the other two. *Grade out of 3? Write "3" here:*
- 2. A long straight wire carrying a current produces a magnetic field. The field magnitude at a point 1 m from the wire is 6 T. If the current in the wire is tripled, then the magnetic field magnitude at a point 6 m from the wire will be:
 - A. 1 T
 - B. 2 T
 - C. 3 T
 - D. 6 T
 - E. 9 T
 - F. 12 T
 - G. 18 T

Grade out of 3? Write "3" here:

- 3. A 2- Ω , a 4- Ω , and an 8- Ω resistor are connected in *parallel* to a battery. Which resistor has the most electrons flowing through it each second?
 - A. the 2- Ω resistor
 - B. the 4- Ω resistor
 - C. the 8- Ω resistor
 - D. All three resistors have the same number of electrons flowing through them each second.
 - E. There is not enough information given to answer this question.
- 4. A uniform 4-tesla magnetic field is present in the boxed region, pointing in the direction indicated on the diagram. A wire in the boxed region is carrying a current of 3 A in the direction shown by the arrow marked *I*. The wire has a length of 4 m. What will be the magnitude and direction of the force on the wire?

