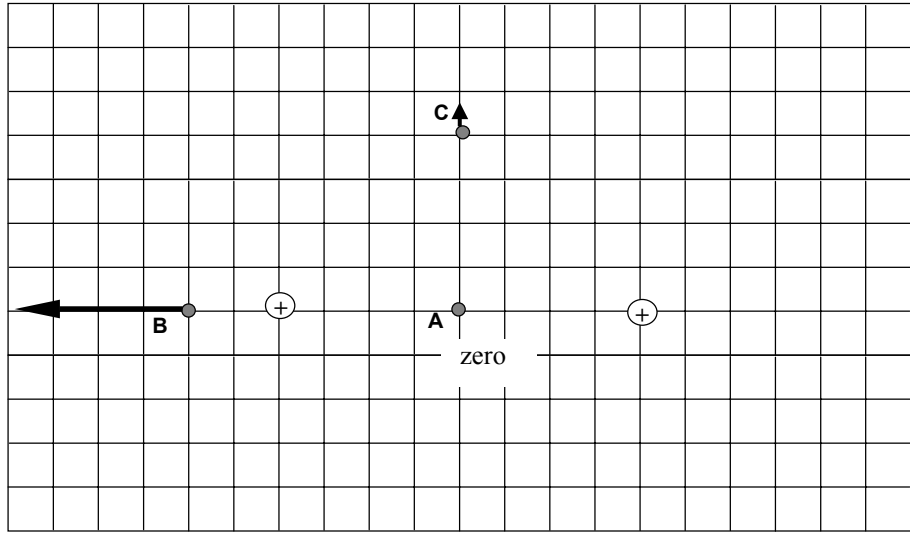


Physics 112: Answers to Exam #2

- I**
- D** Current is larger in both parallel branches than it is in the series circuit; therefore, power dissipated by two-ohm in parallel is larger than power dissipated by two-ohm in series (using $P = I^2R$), and same is true for the five-ohm resistors. In the parallel circuit, ΔV is the same for both resistors, so more power is dissipated in the two-ohm resistor [using $P = (\Delta V)^2/R$].
- D** $\Delta V_{AB} = \Delta V_{bat} = \text{constant}$.
- D** $I_2 = \Delta V_{bat}/R_2 = \text{constant}$.
- A** Initial distance between charges is 5 m, final distance is 4 m.
 $W = \Delta TE = \Delta PE = PE(\text{final}) - PE(\text{initial}) = kQq/r_{\text{final}} - kQq/r_{\text{initial}} = kQq/4 - kQq/5 = (1/20) kQq = (1/4) (kQq/5) = (1/4) (40 J) = 10J$.
- A** The force is toward the north because the electric field points toward lower potential, and is perpendicular to the equipotential lines. The force is stronger at point B because the field is stronger there, as indicated by the tighter spacing of the equipotential lines.
- C** The current through R_3 is 3 A ($=\Delta V_3/R_3$), which is the same as the current throughout the whole segment including point B.
- A = D = E > B = C**
- The potential drop across bulbs A, D, and E is the same (equal to the battery voltage), so the current through all three of them will be the same. The potential drop across bulbs B and C are both equal to half the battery voltage, so the current through those bulbs will be smaller than the other three (but equal to each other).
- A) $I_{R3} > I_{R1} > I_{R2}$ [current splits after going through R_3 , more than half goes through R_1]
B) $\Delta V_3 > \Delta V_1$ because those two resistances are equal, and so potential difference will be proportional to the amount of current through them.
C) $\Delta V_{bat} = \Delta V_3 + \Delta V_1$ and $\Delta V_{bat} = \Delta V_3 + \Delta V_2$, according to Kirchoff's loop rule.

11.



12. $PE = qV = 0 \text{ V}$ at left plate, so gain in PE is one box for a potential change of one volt. Therefore, the charge gains two boxes of PE, and loses two boxes of KE, for each 2-V change in potential as it moves.

