

Addressing Learning Difficulties with Circuits: An “*Aufbau*” Approach

David E. Meltzer
Department of Physics and Astronomy
Iowa State University

* “*Aufbau*” = “building up” as in, e.g., atomic physics.

Research on Learning of Electric Circuit Concepts

- **Pre-college students**
 - Shipstone (1984)
- **Early work with college students**
 - Fredette and Lochhead (1980)
 - Cohen, Eylon and Ganiel (1982)
- **Extended investigations with college students**
 - Shaffer and McDermott (1992)
 - Harrington (1995)

General Conceptual Problems with Circuits

- Students retain confusion with “building block” concepts such as charge, field, potential, etc.
- Students struggle with common ***representations*** of circuits e.g., relating circuit diagrams to drawings, and drawings to actual equipment
- Students do not have separate concepts attached to the words “current,” “power,” “energy,” and “voltage.” (*it’s all “electricity”*)

This exacerbates tendency toward confusion

- “batteries have constant *current*” [instead of *voltage*]
- “*current* gets used up in circuit elements” [instead of *energy*]

The two *most universal* conceptual difficulties regarding circuits:

- Most students believe strongly that electric current gets *used up* as it moves through circuit elements.
- The overwhelming majority of students are ***certain*** that a battery will always produce the same amount of current *regardless of the circuit to which it is attached*.

It is EXTREMELY DIFFICULT to persuade students that these ideas are not correct!

Key Conceptual Obstacles

Before Confronting Circuits

[when using traditional sequence of topics]

- Understanding concept of “*potential*”
- Distinguishing between “*potential*” and “*potential difference*”
- Understanding concepts of “*current*” and “*resistance*”
- Realizing that potential *decreases* as positive charges flow through a resistor
- Recognizing that **energy** (*not current*) is “used up” in resistors
- Realizing that current flow is proportional to *potential* **difference** (*not potential*)
- Recognizing that an “ideal” conducting wire is an equipotential volume

Key Conceptual Obstacles

Specific to Complete Circuits

(related to *global* characteristics)

- Sum of potential changes in a closed current loop equals zero
- (Ideal) battery provides constant potential difference, but **varying** amounts of current
- Current flowing out of battery may “split up” into multiple pathways and then recombine (***to original magnitude***) before re-entering battery

“Current First” Instructional Strategy

(University of Washington, PEG)

[“Physics By Inquiry” and “Tutorials in Introductory Physics”:
Extended hands-on investigations using batteries and bulbs.]

- 1) Introduce concept of complete circuit: *try to light bulb with wire and battery*
- 2) Introduce concept of current: *current not “used up”; current through a battery depends on circuit configuration.*
- 3) Introduce concepts of resistance and equivalent resistance
- 4) Introduce ammeters, voltmeters, and concept of potential difference.
- 5) Finally, introduce concepts of energy and power.

Advantages of “Current First” Strategy

[Cf. Shaffer & McDermott, 1992]

- Avoids need for immediate grappling with “potential” concept.
- Notion of “flow” relatively easy for students to accept.
- Averts probable early confusion of “energy loss” with current “non-conservation.”
- Allows much deduction and model-building based on *qualitative* observation.

→ *But what if there is **no** laboratory
and **no** recitation available?→*

Characteristics of This Course

- Algebra-based general physics course (at Southeastern Louisiana University)
- All activities involved pencil & paper work in lecture hall (group and individual work)
- Laboratory ***not required***; most students took completely traditional laboratory (independent of lectures)

Another Strategy: Emphasis on Potential

*“Workbook for Introductory Physics” by Meltzer and Manivannan; for in-class use without relying on lab. Used **Fall 1997** and **Spring 1998**.*

Both semesters: Extended development of electric forces and fields, electric potential energy, and electric potential;

Fall 1997: Study of **complete** circuits merged with current and Ohm’s law concepts (introduced same day);

Spring 1998: Intensive study of current, “voltage,” and Ohm’s law **before** discussion of circuits; examination of circuit segments “builds up” to complete circuits;

Both semesters: Step-by-step analysis of **very simple** circuits.

Circuit Diagnostic Question Set

(Four-item quiz, with virtually identical questions presented in four different forms [word problem, “math” problem; diagrammatic problem, graphical problem]).

Question #2:

Parallel circuit: *battery* = V volts; $R_A = 6\Omega$; $R_B = 9\Omega$.

Series circuit: *battery* = V volts; $R_C = 7\Omega$; $R_D = 3\Omega$.

Ⓜ A. $\frac{I_B}{I_C} > 1$

C. $\frac{I_B}{I_C} < 1$

B. $\frac{I_B}{I_C} = 1$

D. $\frac{I_B}{I_C} = -1$

Comparative Performance on Four-item Diagnostic

- Fall, 1997 (N= 60)
Mean score out of 4: 2.0 ± 0.2
- Spring, 1998 (N= 58)
Mean score out of 4: 2.8 ± 0.2

[significant improvement, $p < 0.001$]

Other Assessment Questions

- **[Ohm's law]** *Two identical resistors are carrying an electric current; the electric potential at the left end of each resistor is 6 V. The potential at the right end of resistor "A" is 12 V, and the potential at the right end of resistor "B" is 9 V. If 4 A flows through resistor "A," how much current flows through resistor "B"? [Answer: 2 A]*
- **[Series Circuit]** *A 2-ohm resistor and a 1-ohm resistor are connected in series with a 9-V battery. What is the voltage drop across the 2-ohm resistor? [Answer: 6 V]*
- **[Parallel Circuit]** *A 3-ohm, a 6-ohm, and a 9-ohm resistor are connected in parallel with a 6-V battery. Which of the resistors will have the most charges flowing through it each second? [Answer: the 3-ohm resistor]*

Comparative Results on Other Assessment Questions

(given on final exam)


(correct responses)

	Fall 1997 <i>(N = 61)</i>	Spring 1998 <i>(N = 61)</i>
Ohm's law	67%	67%
Series Circuit	79%	84%
Parallel Circuit	89%	90%

Final Assessment Question #1

(given on final exam, Spring 1998)

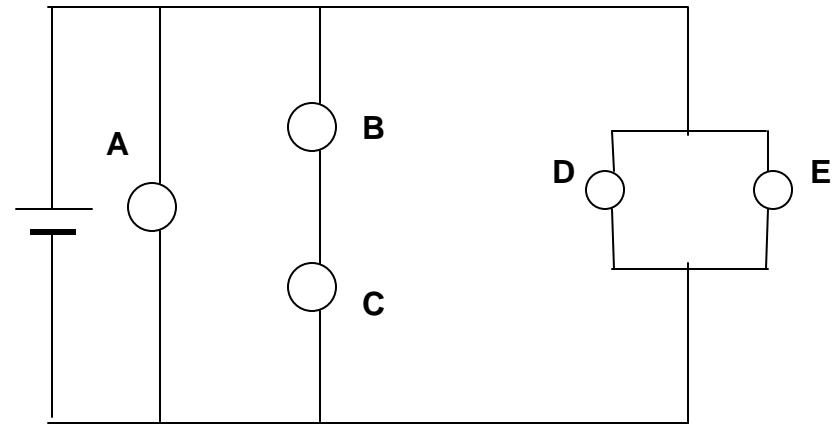The circles in this diagram represent *identical* light bulbs.



Rank, in order, the following:

- A. The brightness of bulb "A"
- B. The brightness of bulb "B"
- C. The brightness of bulb "C"
- D. The brightness of bulb "D"
- E. The brightness of bulb "E"

[Answer: $A = D = E > B = C$]

This class (*algebra-based physics*, $N = 61$):

59% correct responses

Traditional instructional (*calculus-based*):

15% correct responses

[reported by *Shaffer & McDermott*, 1992]


Final Assessment Question #2

(given on final exam, Spring 1998)

The circles in this diagram represent *identical* light bulbs.

Rank, in order, the following:

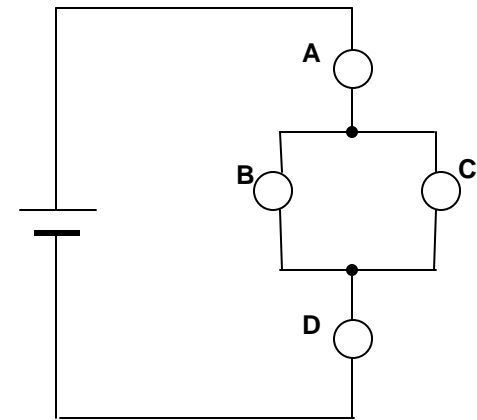- A. The brightness of bulb "A"
- B. The brightness of bulb "B"
- C. The brightness of bulb "C"
- D. The brightness of bulb "D"



Explain your reasoning.

[Answer: $A = D > B = C$]

Results (*algebra-based physics*; $N = 61$):

54% correct with correct explanation;

20% : $A > D$ **because** "the voltage is less at D"

15% : $B = C > A = D$ **because** "B & C are in parallel"

8% : $A = B = C = D$

3% correct with incorrect (or missing) explanation;

Highlights of Assessment Data

(Note: No “bulb brightness” problems given during course; only on final exam)

- Higher rate of correct responses than in traditional instruction (59% vs. 15 % on #1; 54% vs. < 50% on #2)
- 20% of students still reflect “**current gets used up**” misconception – less than in traditional instruction (40%) but more than in tutorial instruction (5-10%)

[Cf. Shaffer and McDermott, 1992; Harrington, 1995]

Summary: Balance Sheet of “*Workbook*” Strategy

Advantages:

- close contact between circuit theory and preceding development of field, force, energy, and potential concepts
- provides an option when lab work is not required or not available

Disadvantages:

- confusion between current and potential may be aggravated
- only very simple circuit configurations are dealt with
- lack of “hands-on” a potentially fatal constraint on understanding